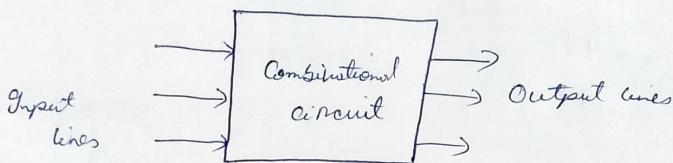


Ch-4 - Combinational logic

Combinational Circuit a type of digital logic circuit whose output depends on the present input values only and does not depend on past output and input values.

- It does not have any feedback path between input and output.
- Open loop system.



- Three key elements
 - Input lines - Enter input values into the combinational circuit.
 - Processing Unit - Main element.
 - Processes the input values depending on the type of circuit.
 - Output lines - Take results generated by the circuit.
- Characteristic of CC -

- The output of a CC at any instance of time, depends only on the present input values at that instant of time.
- CC do not use any kind of memory element in their circuits. Thus they do not store the previous state of input and output.
- The output of CC can entirely predicted using its logical operation and input values.
- CC produce an instantaneous output in response to any change in its input values.

- Types
- (i) Binary Adder \checkmark (ii) Binary Subtraction \checkmark (iii) Multiplexers \checkmark (iv) Demux
 - (v) Encoders \checkmark (vi) Decoders \checkmark (vii) Comparators

Designing of Combinational Circuit:



Step 1: Determine and define total I/P's and total O/P's of the circuit.

Step 2: Make truth table that defines relationship between I/P's & O/P's

Step 3: Determine Boolean eqⁿ using K-map

Step 4: Based on B.T., we can form circuit


Q: The minimal function that can detect "divisible by 2" with 8421

BCD $[D_3 D_2 D_1 D_0]$ is given by $\overline{D_1}$


| | D_3 | D_2 | D_1 | D_0 | y |
|------|-------|-------|-------|-------|-----|
| 0 - | 0 | 0 | 0 | 0 | 1 |
| 1 - | 0 | 0 | 0 | 1 | 0 |
| 2 - | 0 | 0 | 1 | 0 | 1 |
| 3 - | 0 | 0 | 1 | 1 | 0 |
| 4 - | 0 | 1 | 0 | 0 | 1 |
| 5 - | 0 | 1 | 0 | 1 | 0 |
| 6 - | 0 | 1 | 1 | 0 | 1 |
| 7 - | 0 | 1 | 1 | 1 | 0 |
| 8 - | 1 | 0 | 0 | 0 | 1 |
| 9 - | 1 | 0 | 0 | 1 | 0 |
| 10 - | 1 | 0 | X | 0 | X |
| : | | | | | |
| 15 - | 1 | 1 | X | 1 | X |

| $D_3 D_2$ | $D_3 D_2 D_1$ | $D_3 D_2 D_1 D_0$ |
|-----------|---------------|-------------------|
| 00 | 00 | 00 |
| 00 | 01 | 01 |
| 01 | 10 | X ₁₀ |
| 01 | 11 | 11 |
| 11 | 00 | 1 ₀₀ |
| 11 | 01 | 5 |
| 11 | 10 | 13 |
| 11 | 11 | 9 |
| 10 | 00 | 3 |
| 10 | 01 | 7 |
| 10 | 10 | 15 |
| 10 | 11 | 11 |
| 00 | 10 | 1 ₂ |
| 00 | 11 | 16 |
| 01 | 10 | X ₁₄ |
| 01 | 11 | X ₁₅ |

$\overline{D_1}$

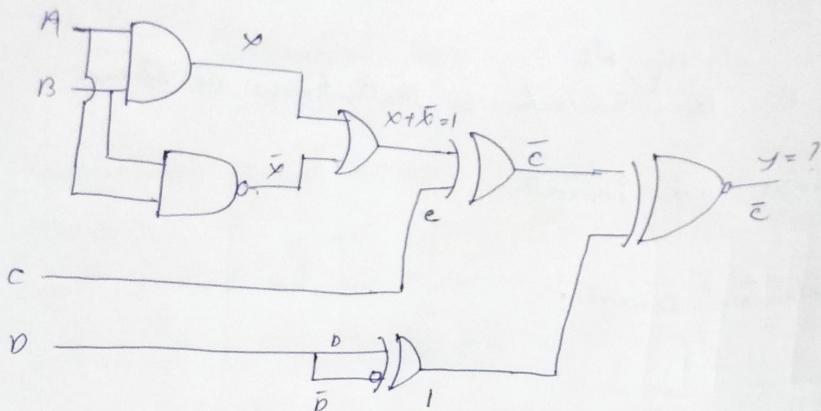

(1)

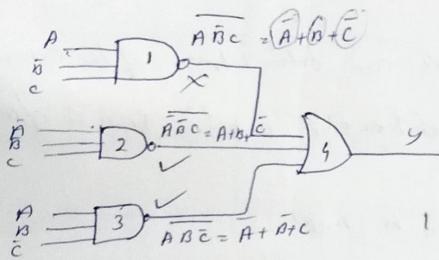


What is redundant gate
in given CC?

1 is redundant -

Check with other gate.. If its present in other gate then
it is redundant gate.


(2)

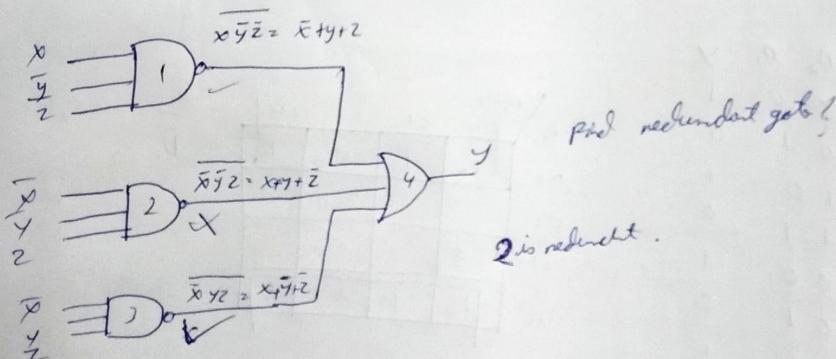

1st redundant gate!

2 is redundant.

②

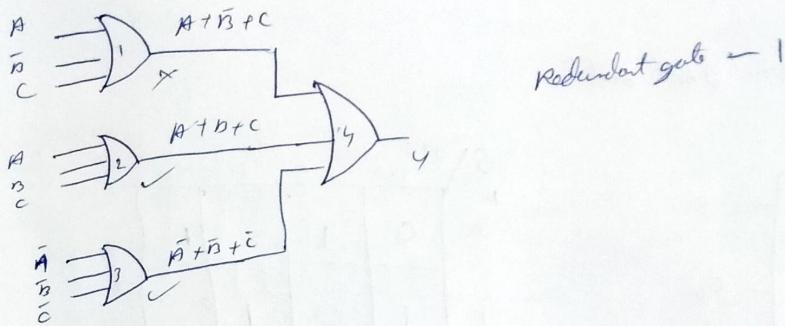Redundant gate $\rightarrow 1$ Half adder:

\Rightarrow If A is a ckt where we perform 2-bit add




| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

| \bar{A} | \bar{B} | S | C |
|-----------|-----------|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


$$\begin{aligned} S &= A\bar{B} + \bar{A}B \\ &= A \oplus B \end{aligned}$$

| \bar{A} | \bar{B} | S | C |
|-----------|-----------|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |

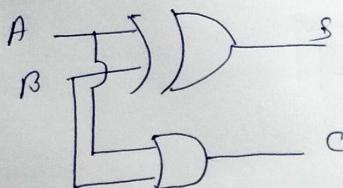

Full Adder

= Used to perform 3 bit add

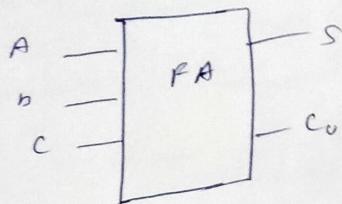


| A | B | C | S | Co |
|---|---|---|---|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| S | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| A | 0 | 0 | 1 | 0 | 1 |
| B | 1 | 1 | 0 | 1 | 0 |
| C | | | | | |


$$\begin{aligned}
 S &= A\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC + \bar{A}B\bar{C} \\
 &= \bar{A}(B\bar{C} + \bar{B}\bar{C}) + A(B\bar{C} + B\bar{C}) \\
 &= \bar{A}(B \oplus C) + A(B \otimes C) \\
 C &= \bar{A}(B \otimes C) + A(\bar{B} \otimes C) = A \otimes B \otimes C
 \end{aligned}$$

| S | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| A | 0 | 0 | 0 | 1 | 0 |
| B | 1 | 0 | 1 | 1 | 1 |
| C | | | | | |

$$C = B\bar{C} + AC + AB$$

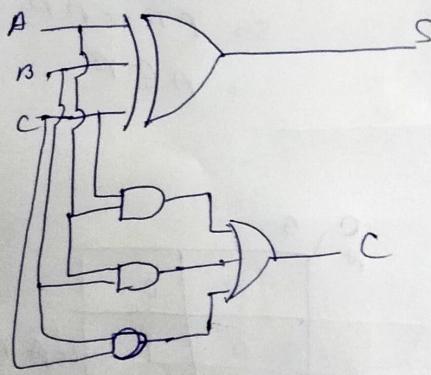

Full Adder using Half Adder

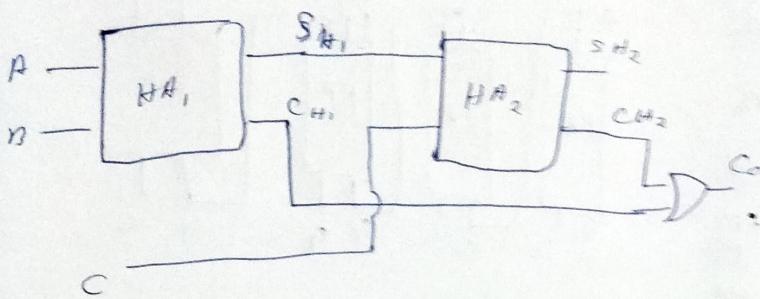

$$A \oplus B = A\bar{B} + \bar{A}B$$

$$S_{H_1} = A \oplus B = A\bar{B} + \bar{A}B$$

$$C_{H_1} = AB$$


$$S_{H_2} = S_{H_1} \oplus C = A \oplus B \oplus C$$

$$\begin{aligned} C_{H_2} &= \neg S_{H_1} \cdot C = (\bar{A}\bar{B} + \bar{A}B)C \\ &= A\bar{B}C + \bar{A}BC \end{aligned}$$

$$\begin{aligned} C_o &= C_{H_2} + C_{H_1} \\ &= AB + A\bar{B}C + \bar{A}BC \\ &= BC + AC + AB \end{aligned}$$

| | | C | | BC | | AB | | A | |
|--|--|----|----|----|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 | 01 | 11 | 10 | 00 |
| | | 0 | | | | 1 | | | 0 |
| | | | | | | | | | |
| | | | | | | | | | |

Half Adder by NAND gates

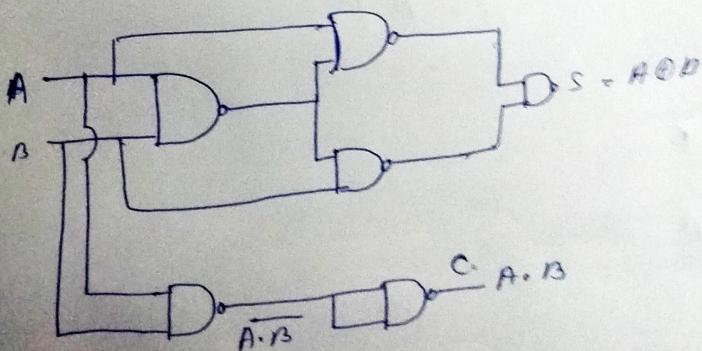


4 Bit Parallel Adder.

| | | | | | | |
|-------|-----|-------|-------|-------|-------|-------|
| A | | C_2 | C_1 | C_0 | | A_0 |
| B | + | B_3 | B_2 | B_1 | B_0 | |
| C_0 | S | C_3 | S_3 | S_2 | S_1 | S_0 |
| | | 3 | 3 | 3 | 3 | 2 bit |
| | | | | | | HA |

↓ ↓ ↓ ↓

FA FA FA HA

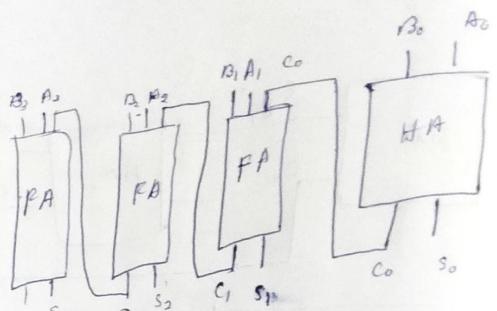

Half Subtraction:

Two bits-

| A | \bar{B} | D | R_3 |
|---|-----------|---|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

| | | |
|---|-----------|---|
| A | \bar{B} | D |
| 0 | 1 | 0 |
| 1 | 0 | 1 |

$$D = A\bar{B} + \bar{A}B$$

$$D = A \oplus B$$

| | | |
|---|-----------|---|
| A | \bar{B} | D |
| 0 | 1 | 0 |
| 0 | 0 | 0 |

$$D = \bar{A}B$$



Full Subtraction

Three bit subtraction.


| A | B | C | D | D_0 |
|---|---|---|---|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| $A \oplus B$ | 00 | 01 | 11 | 10 |
|--------------|----|----|----|----|
| c | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |

$$D = A \oplus B \oplus C$$

| $A \oplus B$ | 00 | 01 | 10 | 11 |
|--------------|----|----|----|----|
| c | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 0 |

$$C = \bar{A}C + \bar{A}B + BC$$

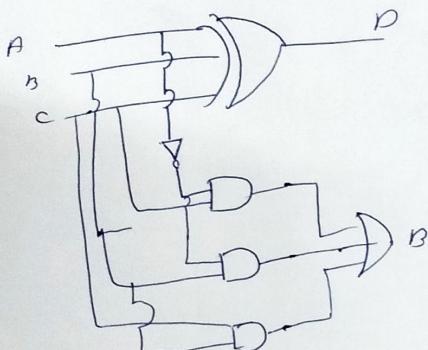

Even Parity / Odd Parity Generation.

Even Parity generator parity = 1, when number of 1's at inputs are ODD.

Odd " "

| b_3 | b_2 | b_1 | b_0 | 0110 (CB even) |
|-------|-------|-------|-------|----------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |

0110 (CB even)

| b_3b_2 | 00 | 01 | 10 | 11 |
|----------|----|----|----|----|
| b_1b_0 | 00 | 0 | 1 | 12 |
| 00 | 0 | 0 | 1 | 8 |
| 01 | 1 | 1 | 0 | 5 |
| 10 | 0 | 1 | 1 | 13 |
| 11 | 1 | 2 | 6 | 14 |

$$P_{\text{even}} = b_0 \oplus b_1 \oplus b_2 \oplus b_3$$

$$P_{\text{odd}} = b_1 \oplus b_2 \oplus b_3$$